

Program: SE

Curriculum Scheme: Revised 2019

Examination: Second Year Semester III

Course Code: ECC/320


Course Name: Electronics devices circuit

Time: 1-hour

Max. Marks: 80


=====  
Note to the students: - All the Questions are compulsory and carry equal marks.


Q1.	If the temperature of a diode increases, then leakage current ..... and Base emitter voltage..... .
Option A:	Increases, Increases
Option B:	Decreases, decreases
Option C:	Decreases, Increases
Option D:	Increases, decreases
Q2.	Load Regulation should be _____ and Line Regulation should be _____ for good power Supply.
Option A:	as low as possible, as high possible
Option B:	as low as possible, as low possible
Option C:	as high as possible, as high possible
Option D:	as high as possible, as low possible
Q3.	In class B push pull Power Amplifier deliver 8W of audio power to output load if transformer efficiency 80%. Calculate Pidc
Option A:	12.73W
Option B:	11.31W
Option C:	13.4W
Option D:	11.13W

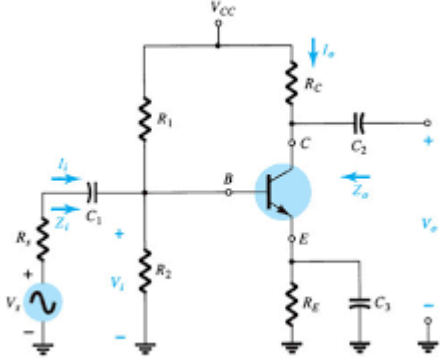Q4.	Heat sink is used in Power transistor to
Option A:	Increase Maximum Power dissipation rating of transistor
Option B:	Decrease Maximum Power dissipation rating of transistor
Option C:	No change in maximum power dissipation rating of transistor
Option D:	Increase/Decrease Maximum Power dissipation rating of transistor
Q5.	Calculate $I_B$ base current and $I_C$ collector current $V_{CC}=9V$ $R_B = 330K\Omega$ $R_C = 1K\Omega$ , $\beta = 100$ for fixed bias circuit.
Option A:	$25.15\mu A$ , $2.5mA$
Option B:	$2.5\mu A$ , $2.5mA$
Option C:	$25.15\mu A$ , $25.15mA$
Option D:	$2.6\mu A$ , $26mA$
Q6.	Calculate the total input capacitance, if amplifier has midrange voltage gain 80, the transistor's $C_{bc}$ is $4pf$ and $C_{be} = 8pf$ .
Option A:	$332pf$
Option B:	$4pf$
Option C:	$8pf$
Option D:	$232pf$
Q7.	For a given circuit if CE capacitor is removed, what is an effect on voltage gain and input impedance. 


Option A:	Voltage gain increases, Input impedance increases
Option B:	Voltage gain decreases, Input impedance increases
Option C:	Voltage gain increases, Input impedance decreases
Option D:	Voltage gain decreases, Input impedance decreases
Q8.	For a given Amplifier Calculate voltage gain, $I_{DSS}=7\text{mA}$ , $V_p=-2.5\text{V}$ $V_{gs}=1.6\text{V}$ , $g_{m0}=5600\mu\text{s}$ , $R_g=1\text{M}\Omega$ , $R_d=2\text{K}\Omega$ , $R_L=10\text{K}\Omega$
Option A:	-3.36
Option B:	4.032
Option C:	20.16
Option D:	5.06
Q9.	Calculate output resistance of an amplifier circuit. (use circuit of Q.8)
Option A:	10KΩ
Option B:	1.667KΩ
Option C:	2kΩ
Option D:	Infinite
Q10.	In class A Power Amplifier power dissipation in transistor under no signal condition is _____.
Option A:	Less

Option B:	More
Option C:	Twice the power dissipation under signal condition
Option D:	Same as Power dissipation under signal condition
Q11.	In CE amplifier RE bypassed if load resistor is given, Voltage gain is given by
Option A:	$\beta RC / r\pi$
Option B:	$-\beta(RC \parallel RL) / r\pi$
Option C:	$-\beta RC / r\pi$
Option D:	$-\beta RC / (r\pi \parallel RL)$
Q12.	Q point is affected by temperature. Temperature dependent parameters are
Option A:	$\beta$
Option B:	VBE
Option C:	ICBO, $\beta$
Option D:	VBE, ICBO, $\beta$
Q13.	BJT is current controlled device
Option A:	IC current depends on IB current
Option B:	IB current depends on IC current
Option C:	IC current depends on VBE voltage
Option D:	IB current depends on VBE voltage
Q14.	To use MOSFET as an amplifier, it should be biased in
Option A:	Saturation Region
Option B:	Ohmic region
Option C:	Linear region
Option D:	Cut off region

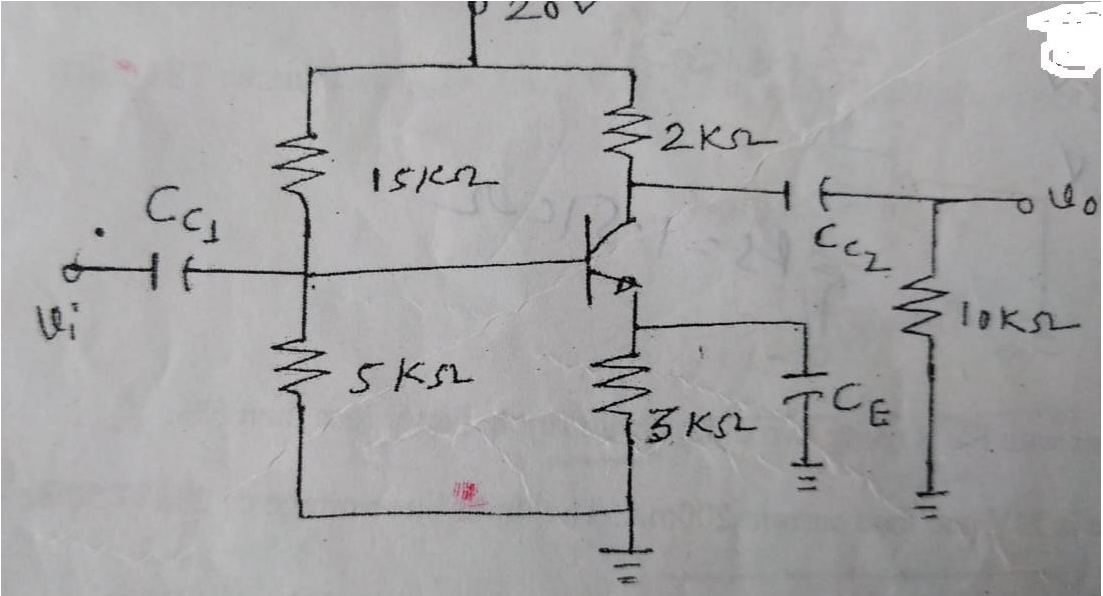
Q15.	<p>For a given Amplifier, calculate voltage gain of an amplifier.  <math>r_{\pi} = 1.5K\Omega</math>, <math>\beta = 120</math></p> 
Option A:	184.61
Option B:	800
Option C:	160
Option D:	190
Q16.	For N channel MOSFET $I_{DQ} = 1mA$ , $K_n = 0.85mA/V^2$ , $V_{TN} = 0.8V$ , Find $V_{GS}$ .
Option A:	1.88V
Option B:	2.3V
Option C:	0.8V
Option D:	0V
Q17.	Calculate $I_B$ for a circuit shown

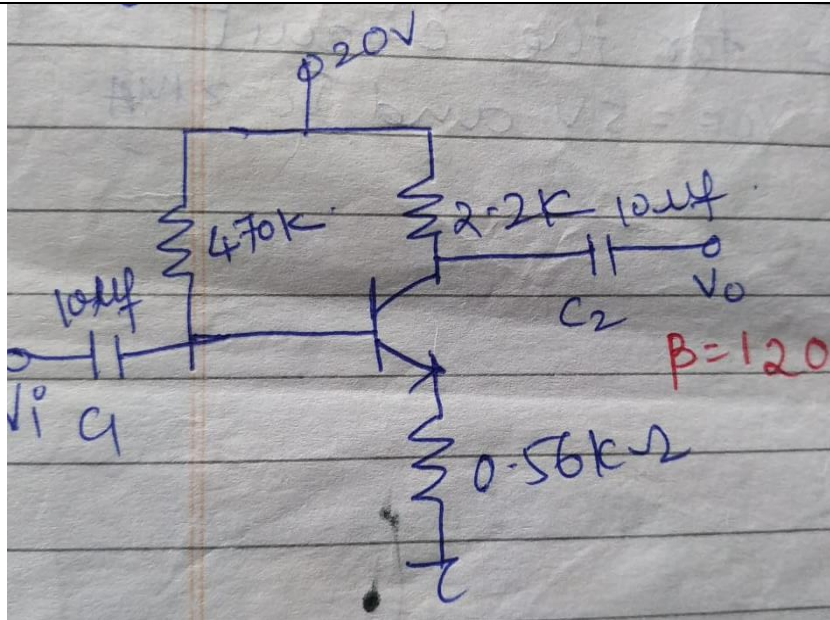

Option A:	33.125µA
Option B:	33.125mA
Option C:	6.625mA
Option D:	6.625 µA
Q18.	Calculate stability factor for given specifications $V_{cc}=9V$ $R_B = 330K\Omega$ $R_C = 1K \Omega$ , $\beta = 100$ for fixed bias circuit.
Option A:	1
Option B:	Infinite
Option C:	100
Option D:	101
Q19.	CMRR can be improved by
Option A:	Increasing differential gain
Option B:	Decreasing differential gain.
Option C:	Increasing common mode gain
Option D:	Decreasing common mode gain

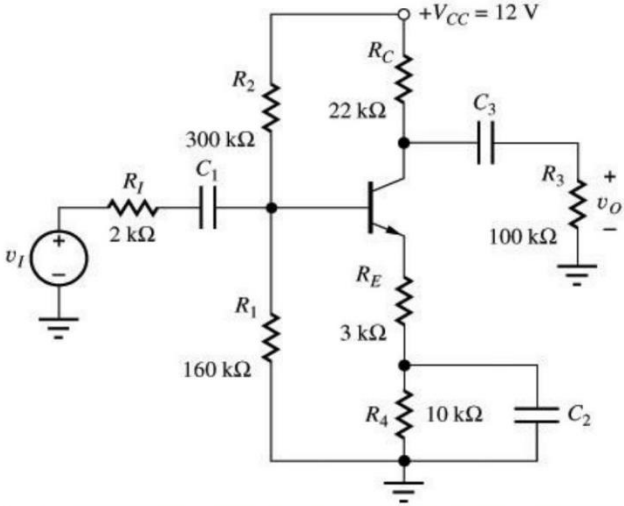
Q20.	<p>Calculate lower cut-off frequency <math>F_{LC3}</math> if <math>C_3=1\mu\text{f}</math> for a given circuit.</p> 
Option A:	0HZ
Option B:	1.3HZ
Option C:	3.1HZ
Option D:	$\infty$ HZ

Q.2 (A)(i)	<p>Explain Frequency response of an amplifier and its significance. For a given circuit if CE capacitor is removed, what is an effect on voltage gain and input impedance.</p>
Q.2 (A)(ii)	<p>For Zener voltage regulator output voltage is 9V from an automobile battery whose voltage may vary between 11V and 13.6V. The current vary between 0mA to 100mA. Find <math>R_s</math> resistor and <math>P_{zmax}</math>.</p>
Q.2 (A)(iii)	<p>Find <math>V_{GS}</math>, <math>V_{DS}</math> for given circuit if <math>I_D = 5\text{mA}</math>. Figure is shown below</p>

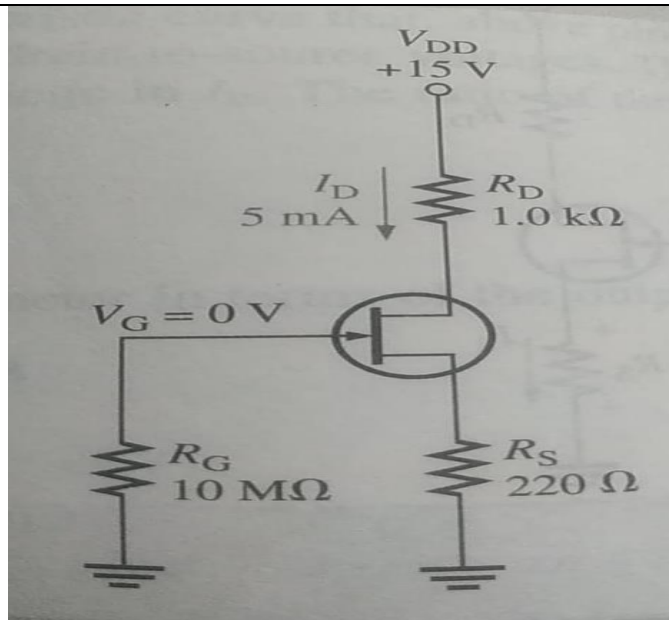

<p>Q.2 (B) (i)</p>	<p>In class B power Amplifier <math>V_{CC}=20V</math>, <math>N_2=2N_1</math>, <math>R_L=20\Omega</math>. The input is sinusoid for maximum output signal at <math>V_{max}=V_{CC}</math> determine</p> <ul style="list-style-type: none"> <li>(i) Output signal power</li> <li>(ii) Collector dissipation in each transistor</li> </ul>
<p>Q.2(B) (II)</p>	<p>Derive voltage gain <math>A_v</math>, current gain <math>A_i</math>, input resistance <math>R_i</math> and output resistance of CE amplifier <math>R_E</math> bypassed.</p>

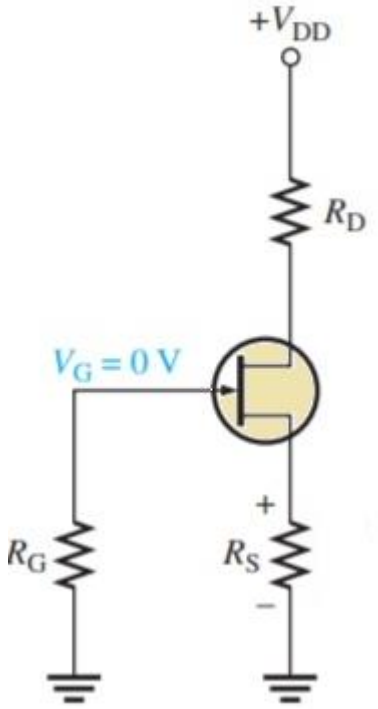

Q.3(A)(i)	State and explain Miller's Theorem.
Q.3 (A)(ii)	<p data-bbox="339 241 1437 315">For the circuit shown find <math>I_D</math> and <math>V_{DS}</math> if <math>V_{RS}=1.5V</math>, <math>R_D=2k\Omega</math>, <math>R_G=1M\Omega</math>, <math>V_{DD}=15V</math>, <math>I_{DSS}=10mA</math>, <math>V_p=-2V</math></p> 
Q.3 (A)(iii)	<p data-bbox="339 1176 1437 1355">In audio system speaker needs 10Watt of output power, calculate <math>P_{Qmax}</math> for transistor for Class A and Class B Power Amplifier. Select a suitable Power Amplifier for Audio system. Give Justification for the answer.</p>
Q.3 (B) (i)	<p data-bbox="339 1364 1437 1438">Explain two transistor(E-MOSFET) constant current source and importance of CMRR.</p>
Q.3(B) (II)	<p data-bbox="339 1447 1437 1520">Determine voltage gain, Input resistance and output resistance for the MOSFET amplifier shown, <math>V_{TN}=0.8V</math>, <math>K_n=1mA/V^2</math>.</p>

